



COMP 3 – 6 (RC)

S.E. (Comp) (Semester – III) (RC) Examination, May/June 2015  
INTEGRATED ELECTRONICS


Duration : 3 Hours

Total Marks : 100

- Instructions :** i) Assume **suitable** data **wherever** required.  
ii) Answer **any five** questions, selecting atleast **one** from **each** Module.

MODULE – I

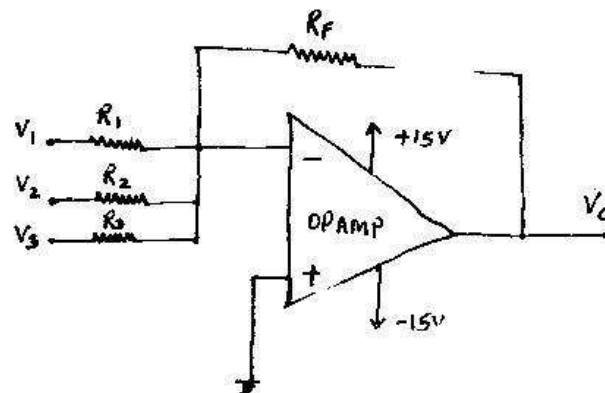1. a) How do ideal OPAMP characteristics differ from that of practical OPAMP characteristics ? Explain. 5
- b) Derive an equation for the closed-loop voltage gain of an OPAMP in a voltage-series feedback amplifier configuration. 8
- c) Describe the working of Schmitt Trigger with neat diagrams and equations. 7
2. a) With respect to OPAMP, describe the following terms : 8
  - i) Input offset current
  - ii) Gain-Band width product
  - iii) CMRR
  - iv) Slew rate
- b) Draw and explain the block diagram of a instrumentation system. 6
- c) i) For the summing amplifier shown below as has following inputs : 6



P.T.O.

**COMP 3 – 6 (RC)**

-2-



$V_1 = 2V$ ,  $V_2 = 3V$ ,  $V_3 = 4V$  and  $R_F = R_1 = R_2 = R_3 = R = 1\text{ k}\Omega$ .

Supply voltages are  $\pm 15V$ . Determine the output voltage.

- ii) With neat circuit diagram, state different characteristics of a voltage-follower circuit.

**MODULE – II**

- |   |     |
|---|-----|
| 3. a) Write a short note on voltage regulator IC LM105.   | 6   |
| b) Explain Monostable multivibrator using timer IC 555.   | 7   |
| c) With neat block diagram, explain the operating principle of phase-locked loop.   | 7 ✓ |
| 4. a) Explain with a neat diagram, how low voltage regulation is achieved using IC723.  | 6   |
| b) Design an astable multivibrator using 555 timer for a frequency of 1kHz and a duty cycle of 70%. Assume $C = 0.1\text{ }\mu\text{F}$ . | 8   |
| c) Describe the following application of PLL :  | 6   |
| i) Phase shifter.   |     |

**MODULE – III**

- |  |     |
|--|-----|
| 5. a) Name the types in Bipolar and Unipolar logic families. Briefly explain.          | 6 ✓ |
| b) Explain the working of a TTL gate. Draw necessary diagram.                          | 6   |
| c) i) Explain the following characteristics of digital IC                              | 4   |
| I) Speed of operation                      II) Noise immunity                          |     |
| ii) Explain CMOS inverter.   | 4   |
| 6. a) Explain the working of a HTL gate. Draw necessary diagram. State its advantages. | 8   |
| b) Draw a neat diagram of modified DTL gate and explain its working.                   | 7   |
| c) State some advantages and disadvantages of a RTL gate.                              | 5   |



MODULE – IV

7. a) Describe 3 bit R-2R ladder D/A converter. State its advantages and disadvantages. 8  
b) Explain with neat diagrams, A/D converter using voltage-to-frequency conversion. 7  
c) Explain some specifications of A/D converter. 5
8. a) Describe Weighted-Resistor D/A converter. State its advantages and disadvantages. 8  
b) Explain with neat diagrams, dual-slope A/D converter. Why such a converter is used in digital voltmeters ? 7  
c) Explain some specifications of D/A converter. 5