



COMP 3 – 5 (RC)

S.E. (Comp.) (Semester – III) (RC) Examination, May/June 2014 LOGIC DESIGN

Duration: 3 Hours

Total Marks: 100

- Instructions:** 1) Answer **five full** questions by selecting **atleast one** question from **each** Module.
2) Diagrams must be drawn **neat and clear** with pencil only.
3) Assume data **if necessary**.

MODULE – I



1. a) Perform the following number conversions : 6
i) $(11.75)_{10}$ to binary
ii) $(8BF4)_{16}$ to octal
iii) $(6327.4051)_8$ to decimal.
- b) Prove the following using Boolean algebraic theorems. 4
 $\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC = AB + BC + CA$
- c) For the following Boolean equation. 6
 $Z = (\bar{C} + D) + \bar{A}C\bar{D} + A\bar{B}\bar{C} + \bar{A}\bar{B}CD + ACD$
i) Simplify the expression to a minimum number of literals using Boolean algebra. Verify the answer using a k-map.
ii) Draw the logic circuit corresponding to this reduced form.
- d) Represent the following decimal numbers in eight bit 4
i) Sign magnitude form
ii) Sign 1's complement form
iii) Sign 2's complement form
1) +27 2) -36
2. a) The Hamming code sequence as received contains error in one position 1101111. Locate the position of error bit using odd parity check. 4
- b) Realize the expression 6
 $(A + C)(A + \bar{D})(A + B + \bar{C})$
using NOR gates only (only 2 inputs).
- c) Minimize the logic function using QM method. 7
 $f(A, B, C, D) = \sum m(0, 1, 2, 8, 10, 11, 14, 15)$
- d) Why 2421 code is called as self complementing code ? Explain with help of example. 3

P.T.O.



MODULE – II

  3. a) What are combinational circuits ? Explain working of a full subtractor using suitable diagrams, k-map and truth tables. 7
- b) Realize the following Boolean expression using a multiplexer with a circuit diagram. 5
- $$f(w, x, y, z) = \sum m(2, 5, 6, 7, 9, 12, 13, 15)$$
- c) It is necessary to multiply two binary numbers each two bits long in order to form their product in binary. Let the two numbers be represented by $a_0 a_1$ and $b_0 b_1$. 8
- Determine the number of output lines required.
 - Find the simplified Boolean expression for each output.
4. a) Explain the working of following latches. 6




- b) Realize a J-K flip flop using D flip flop. Show the conversion procedure. 8
- c) What is race around condition ? Explain any two ways how race around condition can be eliminated. 6

MODULE – III

5. a) Explain the following : 6
- up/down counter
 - Modulus of a counter
 - Lock out of a counter.
- b) The content of a 4 bit shift register is initially 1101. The register is shifted 6 times to right with serial input being 101101. What is the content of the register after each shift. 6
- c) Design a asynchronous decade counter, sketch the output waveform. Make use of J-K flip flops. 8




 6. a) With the help of neat logic circuit and a neat waveform, explain the working of a 3 bit ring counter. What is the modulus of this counter ? 6
- b) Design a 3 bit synchronous up/down counter which counts up when the control signal is $M = 1$ and count down when $M = 0$. 6
- c) Design a synchronous counter with S-R flip flops that goes through the following states. 8



MODULE - IV

 7. a) Explain the steps involved in design procedure for synchronous sequential circuits. 5
- b) For the state diagram shown below obtain the state table and the reduced state diagram with the state table. 8



- c) Show how the PAL circuit is programmed for the following combinational circuit with functions. 7

$$F_1 = AB + AC$$

$$F_2 = AC - BC$$



8. a) A synchronous sequential machine has a single control input x and the clock and two outputs A and B on consecutive rising edges of the clock, the code on A and B changes from 00 to 01 to 10 to 11 and repeats itself if $x = 1$, if at any time $x = 0$ it holds to the present state. Draw the state diagram and implement the circuit using T flip-flops.

8

- b) What are finite state machines ? Explain state table, state diagram and excitation table of R-S flip flop.

6

- c) A combinational circuit is defined by the following functions

$$F_1(A, B, C) = \sum m(3, 5, 6, 7)$$

$$F_2(A, B, C) = \sum m(0, 2, 4, 7)$$

Implement the circuit with a PLA having three inputs, four product terms and two outputs.

6