



## COMP - 3-5 (RC 07-08)

S.E. (Comp) Semester - III (Revised 2007-2008) Examination, May 2009  
**LOGIC DESIGN**

Duration : 3 Hours

Total Marks : 100

*Instructions : 1) Answer five full questions, atleast one from each Module.  
2) Make suitable assumptions, wherever necessary.*

### MODULE - I

1. a) Find the complement of the following boolean function and reduce it to a minimum number of literals  $\overline{B}D + \overline{A}B\overline{C} + ACD + \overline{A}BC$ . 4  
b) For the following function find all of the prime implicants using Quine McCluskey procedure  $f(p, q, r, s) = \sum m(1, 3, 7, 9, 12, 14, 15)$  6  
c) Represent the decimal number 9830 in  
i) BCD  
ii) Excess-3 code 4  
d) Prove that  
i)  $AB + \overline{A}C + A\overline{B}C (AB + C) = 1$   
ii)  $AB + A(B + C) + B(B + C) = B + AC$  6
2. a) Determine the single error correcting code for the information code 10110 for odd parity. 6  
b) Find the minimum sum of products expression for the following function using K map  $f(w, x, y, z) = \sum m(0, 1, 5, 8, 12, 14, 15) + \sum d(2, 7, 11)$  6  
c) Convert the following hexadecimal numbers to decimal  
i) A08F . EA  
ii) 2EB7 4  
d) Realize EX-OR operation using only NOR gates. 4

P.T.O.





## MODULE - II

3. a) Design the circuit of a 3 bit parity generator and the circuit of a 4 bit parity checker using an odd parity bit. 8
- b) What is meant by excitation table of a flip flop? 2
- c) Construct a 16 to 1 line multiplexer using 2 to 1 line and 4 to 1 line multiplexers. 6
- d) Explain the operation of edge triggered S-R flip flop. 4
4. a) Draw the logic diagram of a 2 to 4 line decoder with only NOR gates. Include an enable input. 6
- b) What are the various methods used for triggering flip flop? 4
- c) Realize the following boolean expression using an 8 to 1 line MUX, where w, x and y appear on select lines  $S_2$ ,  $S_1$  and  $S_0$ , respectively  

$$f(w, x, y, z) = \sum m(2, 5, 6, 7, 9, 12, 13, 15).$$
 6
- d) Convert J-K flip flop to S-R flip flop. 4


## MODULE - III

5. a) Design a decade counter to count in excess 3 code sequence. Use minimum number of J-K flip flop. 8
- b) Discuss briefly different types of shift registers. 8
- c) How many clock periods are required to shift a 8 bit number in to 8 bit register? Also show the waveform. 4
6. a) Design a 3 bit synchronous counter using S-R flip flops. 6
- b) Explain how counter can be used as frequency divider. 4
- c) Give some applications of shift registers. 4
- d) Explain the operation of a twisted ring counter and give its state diagram. 6



## MODULE - IV

 7. a) Design a sequential circuit for the following state diagram using R-S flip flops. 8



- b) A sequential circuit has 3 D-flip flops A, B, C and one input x. It is described by following flip flop input function.

$$D_A = (BC' + B'C)x + (BC + B'C')x'$$

$$D_B = A$$

$$D_C = B$$

- Derive the state table for the circuit.
  - Draw two state diagram one for  $x = 0$  and other for  $x = 1$ .
- c) Differentiate between PAL and FAPL.





8. a) Reduce the number of states in the following state table and tabulate reduced state table.

Present State	Next $x = 0$	State $x = 1$	Out put	
			$x = 0$	$x = 1$
a	f	b	0	0
b	d	c	0	0
c	f	e	0	0
d	g	a	1	0
e	d	c	0	0
f	f	b	1	1
g	g	b	0	1
h	g	a	1	0

- b) Show how FPLA circuit can be programmed to implement sum and carry output of a full adder.
- c) What are advantages of
- State diagram.
  - State table.
- d) Design a 3-bit counter which counts in the following sequence  
 $0 - 2 - 5 - 3 - 4 - 0 \rightarrow 2 \dots$