



S.E. (Computer Engineering) (Semester – III) (RC)

Examination, November/December 2015

INTEGRATED ELECTRONICS

Duration : 3 Hours

Total Marks : 100

Instructions : 1) Answer **any five** questions, attempt atleast **one** question from **each** Module.

2) Draw **neat** diagrams if **required**.

3) Assume suitable data if **necessary**.

4) Write description for the questions based on the marks **allotted**.

MODULE – I

1. a) What is the CMRR of an ideal Op-Amp ? 2
b) Draw and explain block diagram of a instrumentation system and name 2 instrumentation Op-Amp IC's. 7
c) Draw the block schematic of an Op-Amp and explain the function of each block. 5
d) Derive output voltage for differentiator with its circuit diagram. 6
2. a) Draw and explain integrator circuit and draw necessary waveforms. What do you mean by 'practical integrator' ? 7
b) What is a feedback ? List 2 types of feedback. Which type is used in linear applications ? Give block diagram representation of current series and voltage shunt feedback. 6
c) With the help of relevant circuit diagram, explain the working of Op-Amp inverting amplifier. Derive expression for voltage gain, input and output resistance. 7

P.T.O.



MODULE – II

3. a) Explain what is meant by 4
- a) Capture range
 - b) Lock range of a PLL.
- b) Explain the working of timer 555 in monostable mode. Draw the circuit and derive necessary equations. 8
- c) Give pin description of LM 105 with its block diagram. 8
4. a) With a neat diagram and relevant waveforms, explain the working of a free running multivibrator using IC 555. Obtain the expression for the time period. 7
- b) Explain how timer 555 can be used as a frequency divider and pulse stretcher. 7
- c) Design a voltage regulator using IC 723 for the following specifications : 6
- $V_o = 5V$, $I_o = 50 \text{ mA}$, $V_{in} = 12 \text{ V}$, $I_{sc} = 75 \text{ mA}$, $V_{sense} = 0.65 \text{ V}$.

MODULE – III

5. a) Explain with a neat circuit diagram working of CMOS Nand gate. List some characteristics of CMOS circuit. 6
- b) Explain why DCTL is not popular in IC technology, although it is simpler than RTL. 6
- c) Draw a neat diagram of 3-input HTL Nand gate driving N similar gates. Explain the working operation of the circuit. Describe its various characteristics, which are related to its better performance. 8
6. a) Explain the working of 2 input DTL Nand gate and draw the circuit for 3 input modified DTL gate. 6
- b) Draw the circuit diagram of 2 input TTL Nand gate and explain its operation clearly stating the conditions of the transistors in the circuit for all possible input combinations. 8
- c) List the characteristics of CMOS and name the types in bipolar and unipolar logic families. 6



MODULE – IV

7. a) Discuss the advantages and disadvantages of R-2R ladder over binary weighted resistor DAC. 5
- b) Explain the voltage to frequency converter and derive the necessary expressions. 5
- c) Draw the circuit diagram of weighted-resistor D/A converter and give uses of A/D and D/A converters. 8
- d) State the advantages of Dual Slope A/D converter. 2
8. a) A D/A converter has a full scale analog output of 10 V and accepts 6 binary bits as input. Find the voltage corresponding to each analog step. 4
- b) Draw the circuit of an 8 bit R-2R Binary ladder. Explain its working as a digital to analog converter. If the logic levels are given by 5 V and 0 V for logic one and logic zero respectively, calculate the output voltage when the input is 00100000 ? 10
- c) Define the following terms : 6
- i) Monotonicity
 - ii) Settling time
 - iii) Linearity error.
-