

**S.E. (Comp.) (Semester – III) Examination, Nov./Dec. 2009****LOGIC DESIGN**

Duration : 3 Hours


Total Marks : 100

Instructions : 1) Answer 5 full questions at least one from each Module.
2) Assume any necessary data.

Module – I

1. a) Convert the number $AOOA_H$ into
 - i) Decimal
 - ii) Octal
 - iii) Binary
 - iv) BCD4
- b) Perform the following operations
Add $(-17)_{10}$ to $(-21)_{10}$ using 2's complement method. 4
- c) Suppose the Hamming code sequence 1101011 is transmitted and due to error in one position it is received as 1101111. Locate the position of error bit using add parity check. 4
- d) Prepare a K-map for function
 $F = AB + A\bar{C} + C + AD + A\bar{B}C + ABC$.
Minimize it and realise the minimized equation using Nand gates only. 6
- e) What do you mean by Duality ? Give an example. 2
2. a) Prove the following using Boolean Algebra
 - i) $(A + B)(B + C)(C + A) = AB + BC + AC$
 - ii) $AB + \bar{A}C = (A + C)(\bar{A} + B)$.6
- b) Simplify the Boolean expression using Q-M method
 $f(A, B, C, D) = \sum_m(3, 5, 8, 10) + d(1, 4, 6)$. Design/draw logic circuit using NOR gates only. 8
- c) Why gray code is called as a reflected code ? Explain Binary to Gray and Gray to Binary conversion of a 4 bit binary number with suitable examples. 6

P.T.O.


 


Module – II

3. a) A certain application requires that the absence of input pulses (Constant low) on two input lines can be indicated by a high output. The condition in which both inputs have simultaneous, Positive pulse must also be indicated by a high output. Draw the logic diagram for this circuit.

Support your answer with a truth table.

  - b) Explain the working of the following latches.



- c) Convert a D flipflop to a JK flipflop.

- d) Design a 8 bit adder-subtractor circuit and explain its working with the help of a diagram.

4. a) Explain positive and negative edge triggered flipflops.

- b) It is necessary to multiply 2 binary numbers, each 2 bits long in order to form their product in binary. Let the 2 numbers be represented by a_0a_1 and b_1b_0 .

i) Determine no. of o/p lines required

ii) Find the simplified Boolean expression for each output.

- c) Implement the following function using a multiplexer

$$F(A, B, C, D) = \sum (0, 1, 3, 4, 8, 9, 15).$$

- d) Design a circuit for code conversion from excess – 3 to binary coded decimal. Assume 3 bit input.




Module – III

5. a) Explain the following :
- i) Ripple counter
 - ii) Modulus of a counter and the terminal count
 - iii) Lockout of counter.
6. b) The content of a 4 bit shift register is initially 1101. The register is shifted 6 times to the right with serial input being 101101. What is the content of the register after each shift ?
- c) Design a counter using T flipflop that generates the following binary sequence 0, 1, 3, 7, 6, 4 and repeat .
- d) Write the different applications of a shift registers.
6. a) Design a mod-6 synchronous counter using JK flipflops.
- b) Design and explain the working of a 4 bit bidirectional register.
- c) Write a count sequence of a 3 bit binary down counter. Design a ripple counter using flipflops for this sequence.


Module – IV

 7. a) For the state diagram shown below design the circuit using SR flipflop.





 - b) Design a sequential circuit which tests 3 consecutive bits in a bit stream. If 3 consecutive bits are 1 then the output of the sequential circuit should be active. 6
- c) How does PLA differ from a ROM? 4
8. a) Obtain the state table for the following. 4



- b) Design a serial adder that has 2 input lines X_1 and X_2 and 2 output lines sum and carry. The serial adder has 2 states A and B. It remains in state A if no carry is generated and goes to state B when a carry is generated. Draw the state diagram of the adder and design a suitable circuit using D flipflops. 8
- c) Show how FPLA circuit would be programmed to implement
- $$F_1 = A\bar{B}C + AB\bar{C}$$
- $$F_2 = ABC\bar{B}C + \bar{A}BC + A\bar{B}C$$
- $$F_3 = \bar{A}B$$
- d) Differentiate between Mask programmable PLA and field PLA. 2