

23/12/14 - M.  
Ragunathan



### COMP 3 – 6 (RC)

#### S.E. (Comp.) (Semester – III) (RC) Examination, Nov./Dec. 2014 INTEGRATED ELECTRONICS


Duration : 3 Hours

Total Marks : 100

- Instructions :** i) Assume suitable data **wherever** required.  
ii) Answer **any five** questions, selecting at least **one** from **each** Module.

#### MODULE – I

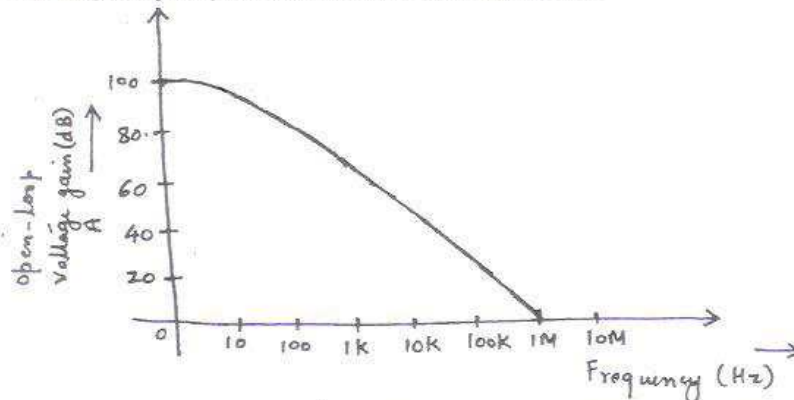1. a) Describe different open-loop configurations of an Op-amp. 8  
b) Derive an equation for the input resistance of an OPAMP with feedback in a voltage-series feedback amplifier configuration. 6  
c) Give comparison between :  
Integrator circuit and differentiator circuit built using OPAMP. 6
2. a) Derive an equation for the  $V_{ab}$  i.e. voltage across the output terminals of the transducer bridge, for the differential instrumentation amplifier. (Assume the use of "resistive transducer" in a bridge). 8  
b) Write a short note on :  
Zero crossing detector using OPAMP. 6  
c) i) The frequency response of IC 741 C is shown below : 3



Determine the voltage gain that can be used to have a maximally flat response at 1 KHz.

- ii) The output voltage of a certain OPAMP circuit change by 20 V in 4  $\mu$ s. What is its slew rate ? 3

P.T.O.



## MODULE – II

- |   |     |
|---|-----|
| 3. a) List various characteristics of a voltage regulator IC LM105.   | 6   |
| b) With a neat functional diagram, explain the timer IC555.   | 7   |
| c) Explain with neat diagram, phase-locked loop.  | 7   |
| 4. a) Differentiate between :<br>High voltage regulator using IC723 V/s Low voltage regulator using IC723.                            | 6   |
| b) Design an astable multivibrator as a square wave oscillator. Draw the neat circuit diagram, equations derived and output waveform. | 8 ~ |
| c) Describe the following application of PLL :<br>i) FM detector.   | 6   |

## MODULE – III

- |  |   |
|--|---|
| 5. a) What are logic families ? Describe its different types.  | 6 |
| b) Explain the working of a RTL gate. Draw necessary diagram.  | 6 |
| c) i) State and explain any two characteristics of digital IC.   | 4 |
| ii) Explain the working of a CMOS Inverter.  | 4 |
| 6. a) Explain the working of a DTL gate. Draw necessary diagram. How is it different from a modified DTL gate ? Explain. | 8 |
| b) Draw a neat diagram of a ECL gate and explain its working.  | 7 |
| c) State some advantages and disadvantages of a TTL gate.  | 5 |

## MODULE – IV

- |  |   |
|--|---|
| 7. a) Explain giving examples where A/D and D/A converters are used.   | 6 |
| b) Describe A/D converter using Voltage-to-Frequency conversion. What is the use of monostable multivibrator circuit in it ? | 8 |



- c) Briefly explain the following specifications for D/A converter : 6
- i) Resolution
  - ii) Linearity
  - iii) Accuracy
  - iv) Settling time.
8. a) Differentiator between weighted-resistor D/A converter and R-2R Ladder D/A converter. 6
- b) Describe Dual-slope A/D converter. Carry out the analysis for the output of the counter w.r.t. its working functionality. 8
- c) Explain some specifications of A/D converter. 6