



F.E. (Semester – II) Examination, May/June 2013

BASIC ELECTRONIC ENGINEERING

(Revised 2007-08)


Duration : 3 Hours

Total Marks : 100

- Instructions :** 1) Answer **five** questions, choosing atleast **one** from **each** Module.
2) Assume any additional data, if **required**.
3) Graph papers will be provided on **request**.

MODULE – I

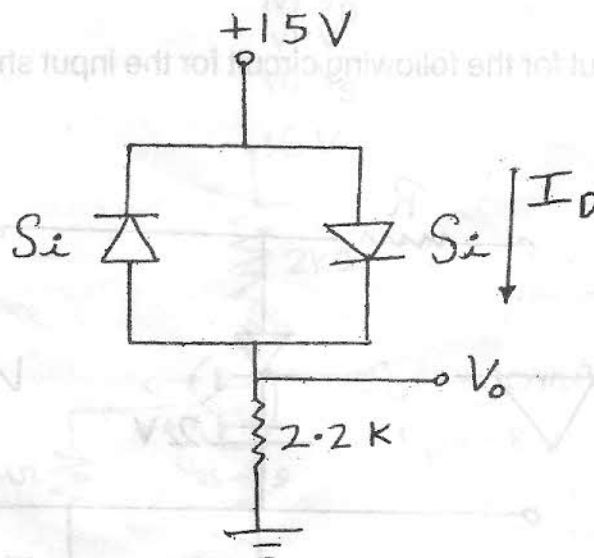1. a) Draw the V-I characteristics of a p-n junction diode and show how the dynamic resistance of the diode can be determined. 4
- b) Differentiate between Zener breakdown and Avalanche breakdown. 4
- c) What is transition capacitance of a diode ? Explain where it is used. 4
- d) Find V_O and I_D for the given circuit. 2



- e) Derive the transformer utilization factor for a half-wave rectifier and compare its value with that of a full-wave bridge rectifier. 6

P.T.O.



2. a) In a center-tap full wave rectifier, $R_L = 1 \text{ k}\Omega$ and each diode has a forward biased dynamic resistance $r_f = 10 \Omega$. The voltage across each half of the secondary winding $= 220 \sin \omega t$. Determine :

i) I_m ii) I_{dc} iii) I_{rms} iv) ripple factor


5

- b) Draw the circuit and input and output waveforms of a capacitor filter. Discuss the effect of the resistance and capacitance values chosen, on the output waveform.

4

- c) For the Zener diode network shown, determine V_L and I_Z .

3

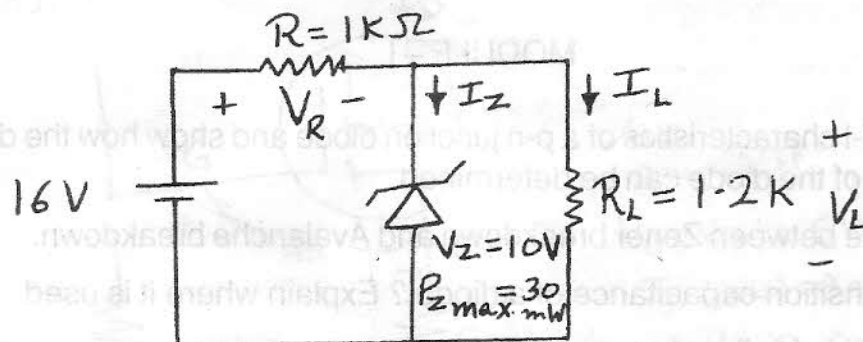


- d) With the help of a neat diagram, explain the working of an unbiased positive clamper and draw the input and output waveforms for a 12 V_{p-p} sinusoidal input.

5

- e) Determine the output for the following circuit for the input shown. Assume ideal diode.

3

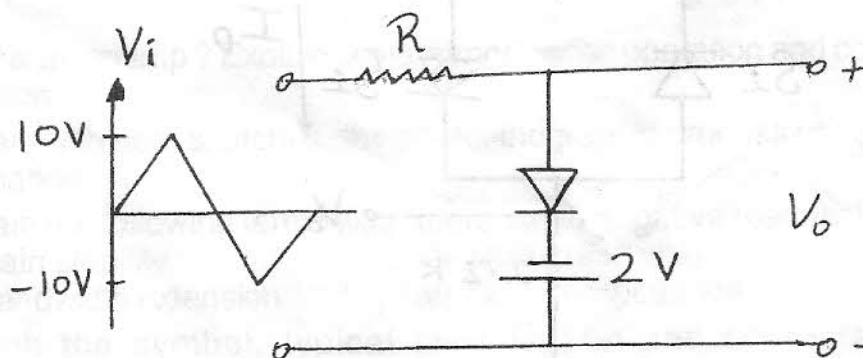

MODULE – II

3. a) Distinguish between the emitter, base and collector regions of a transistor. Derive the relationships between the current gains of Common Base (CB) and Common Emitter (CE) transistors.


6



- b) With the help of a circuit and waveforms, explain how a transistor can be used as an amplifier. Obtain the expression for voltage gain. 8
- c) Draw the circuit setup and explain how the static input characteristics of a CE (npn) transistor are plotted. 6
4. a) Using neat sketches and equations, explain how the graphical load line analysis is employed to determine the operating point for a CE (npn) transistor having emitter bias resistor. 6
- b) With neat diagrams, analyze the following BJT biasing configurations using suitable mathematical expressions and compare the two techniques. Assume the transistor in CE mode.
- i) Fixed Bias ii) Voltage Divider Bias. 8
- c) With the help of a sketch, define the time intervals of a pulse waveform encountered in a switching transistor. 6

MODULE - III

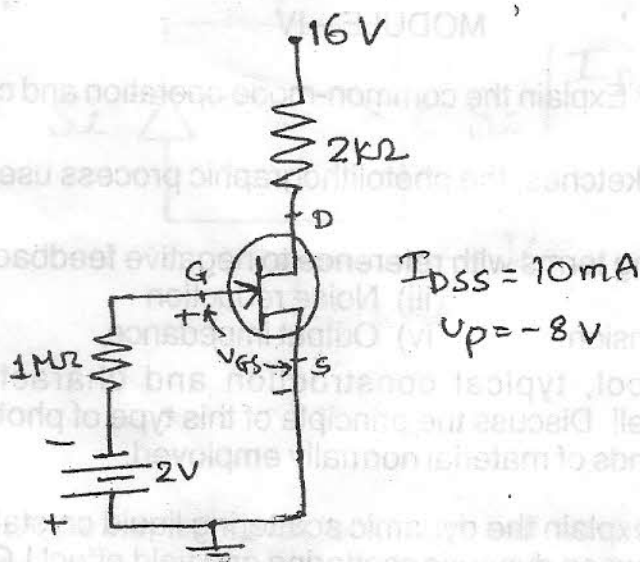5. a) i) Draw the basic construction of a p-channel JFET. 2
- ii) Apply the proper biasing between drain and source and sketch the depletion region for $V_{GS} = 0V$ and $V_{DS} > 0$. 7
- b) Determine the following for the network of fig. below : 7
- i) V_{GSQ} iv) V_D
- ii) I_{DQ} v) V_G
- iii) V_{DS} vi) V_S




- c) Sketch the transfer and drain characteristics of an n-channel depletion type MOSFET with $I_{DSS} = 12\text{ mA}$ and $V_P = -8\text{ V}$ for a range of $V_{GS} = -V_P$ to $V_{GS} = 1\text{ V}$. 6



6. a) Explain in your own words, why the application of a positive voltage to the gate of an n-channel depletion type MOSFET will result in a drain current exceeding I_{DSS} . 7

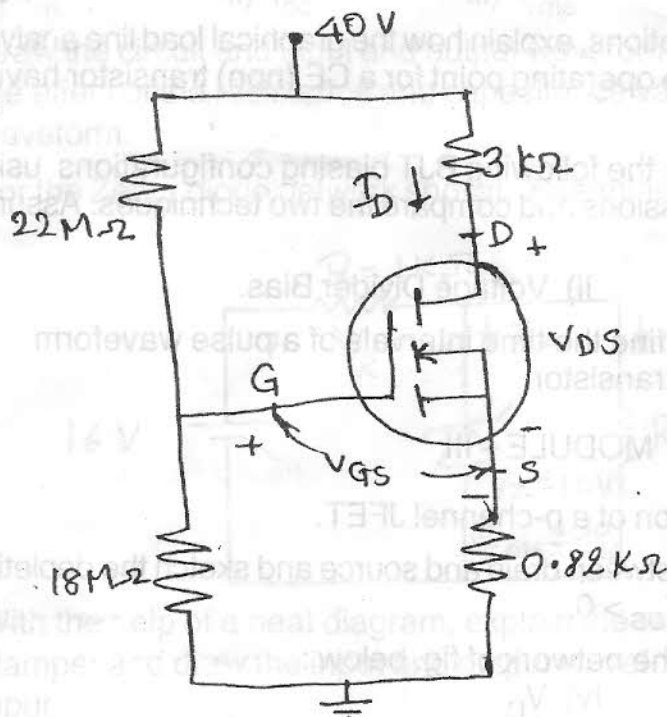b) Determine I_{DQ} , V_{GSQ} and V_{DS} for the network of fig. given below : 7



c) Write short note on CMOS inverter. 6

MODULE – IV

7. a) What is an opamp ? Explain the common-mode operation and common-mode rejection. 6

b) Explain with neat sketches, the photolithographic process used in IC fabrication. 5

c) Explain the following terms with reference to negative feedback : 4

- | | |
|-------------------------|-----------------------|
| i) Gain stability | iii) Noise reduction |
| ii) Bandwidth extension | iv) Output impedance. |

d) Sketch the symbol, typical construction and characteristics of a photoconductive cell. Discuss the principle of this type of photocell and comment on the kinds of material normally employed. 5

8. a) Using illustration, explain the dynamic scattering liquid crystal display. Give the differences between dynamic scattering and field effect LCSs. 7

b) Sketch typical SCR forward and reverse characteristics. Identify all regions of the characteristics and define all important current and voltage levels. 7

c) Write a short note on thermistors. 6