

[Total No. of Questions : 8]

S.E. (Comp.) (Semester - III) (RC) Examination, Nov./Dec. - 2011
INTEGRATED ELECTRONICS


Duration : 3 Hours

Total Marks : 100

- Instructions :** 1) Answer any five questions, at least one question from each module.
 2) Make suitable assumptions, wherever necessary.

MODULE - I

 - Q1)** a) Derive equation for input and output resistance with feedback in voltage series feedback amplifier. [9]
 b) Draw and explain block diagram of an instrumentation system and name two instrumentation opamp ICs? [6]
 c) What are the electrical characteristics that op-amp (ideal) should display? [5]
- Q2)** a) What are compensating networks? Why are they required? [5]
 b)



- In the above fig. if $\pm V_{sat} = \pm 13V$, find V_{UT} and V_{LT} if $V_i = 5 \sin \omega t$, find the wave form of the output voltage. Why schmitt trigger is called as regenerative comparator. [7]
- c) Derive equation for summing, weighted, Averaging amplifier along with a circuit diagram in inverting configuration. [8]

MODULE - II

- Q3)** a) Explain design of low voltage regulator using IC 723. Draw the circuit and write relevant equations. [6]
 b) Explain how IC 555 timer can be used as a Astable operation along with a circuit & equation. [8]
 c) Draw a neat block diagram and explain working of PLL. [6]

P.T.O.

- Q4) a) Explain how timer 555 can be used as a frequency divider & pulse stretcher. [7]
b) Explain any two applications of PLL. [7]
c) Explain series voltage regulator along with a circuit and give pin configuration of LM 105. [6]

MODULE - III

- Q5) a) Explain with a neat diagram the working of 3-input DTL NAND gate. Also draw the circuit for modified DTL gate. [9]
b) Describe the 3-input HTL NAND with fanout of 'N' similar gates and give its advantages. [7]
c) Give a symbol for CMOS transmission gate and along with a circuit its operation. [4]
- Q6) a) Explain with a neat diagram the working of 2-input CMOS NOR gate. [6]
b) What are the modifications in incorporated TTL, to overcome the limitation of speed compared to DTL. [3]
c) Explain wired-OR connections and fanout in ECL gates. Name two popular ECL families. [7]
d) Name the types in Bipolar and unipolar logic families. [4]

MODULE - IV

- Q7) a) Explain A/D converter using voltage to frequency converter, along with schematic and waveforms. [8]
b) Describe 3 bit R-2R ladder D/A network. State its advantages & disadvantages. [8]
c) What is the conversion time of a 10-bit successive approximation type A/D converter using a 1MHz clock and define conversion time of A/D converter. [4]
- Q8) a) A 8-bit DAC has a resolution of 20 mV/bit, what is the analog output voltage for the following digital input codes. [6]
i) 11100011 ii) 11111100
b) Give some examples where A/D & D/A converters are used. [6]
c) Explain successive approximation A/D conversion process and along with the effect of offsetting the scale in successive approximation weighing. [8]

