



S.E. (Comp.) (Sem. III) (RC) Examination, May 2010

INTEGRATED ELECTRONICS

Duration: 3 Hours

Total Marks: 100


Instructions : 1) Answer 5 questions by selecting atleast one from each Module.

2) Answers to subquestions of a question should be written in continuation of each other.

3) Make suitable assumptions wherever necessary.

MODULE – 1

 1. a) Define the following electrical parameters input offset voltage, input resistance CMRR and slew rate. 6
- b) What is a feedback ? List two types of feed back ? Which type is used in linear applications ? Give block diagram representation of current series and voltage shunt feedback. 6
- c) Draw the circuit diagram of an opamp configured in the inverting mode as a summing scaling and averaging amplifier. Derive an expression for the O/P. 8
2. a) With the help of a neat diagram, explain how opamp can be used as differentiator. Show the output wave forms for square and sine wave inputs and draw the frequency response. 8
- b) For the Schmitt trigger circuit shown below, find the upper and lower Trigger points if $R_1 = 100\Omega$, $R_2 = 50K\Omega$ and the supply voltages are $+15V$ and $-15V$. 4



- c) Draw and explain block diagram of a instrumentation system and name the IC number of its. 8



MODULE – 2

3. a) Explain how IC 555 can be used as a astable multivibrator and obtain the expression for the frequency. 8
- b) Design a low voltage regulator for the following specifications. $V_0 = 5V$, $I_m = 50mA$, $V_{in} = 15V$, $T_A = 25^\circ C$, $V_{sense} = 0.65V$. 4
- c) Explain the working of PLL and give one application with explanation. 8
4. a) Give pin description of LM105 with its block diagram. 8
- b) Explain the applications of mono stable multivibrator (any 2). Why it is called as one shot multivibrator ? 8
- c) Give basic principle of series voltage regulator. 4

MODULE – 3

5. a) Draw the circuit diagram to show how DCTL gates can be connected to perform the logic operation AND and NOT. 4
- b) Explain the following with respect to digital logic circuit.
 - 1) Noise margin
 - 2) Propagation time delay
 - 3) Current source logic. 5
- c) Draw the circuit diagram of 2 – input TTL NAND gate and explain its operation clearly stating the conditions of the transistors in the circuit for all possible input combinations. 8
- d) Compare the current spikes in ECL and TTL gates. 3
6. a) What are the advantages of CMOS family over other logic families ? Draw and explain the working of a CMOS inverter. Verify the operation is performed for all input combinations. 6
- b) Calculate :
 - 1) Noise margin
 - 2) Fanout
 - 3) Power-dissipation of HTL gate.

Assume $h_{FE} = 40$

Draw the circuit diagram of HTL gate. 6



c) Compare the following logic families :

- 1) DTL
- 2) HTL
- 3) TTL
- 4) ECL.

8

MODULE – 4

7. a) Explain analog to digital converter using voltage to time conversion with suitable diagram. Mention its advantage and disadvantage.

8

b) Explain successive approximation type A/D converter and its advantages.

6

c) A D/A converter has a full scale analog output voltage of 10V and accepts six binary bits as input and find the voltage corresponding to each analog step. Explain in detail.

6

8. a) A dual slope A/D converter has a resolution of 12 bits. If the clock rate is 100Hz, what is the maximum rate at which samples can be converted ?

4

b) Draw the circuit diagram and graph of output versus input of following converter

1) Binary weighted resistor network

2) R-2R resistor network.

explain the working of R-2R DAC.

10

c) Define the following terms :

6

1) Monotonicity

2) Settling time

3) Linearity error.