



**S.E. (Comp.) Sem. – III (RC) Examination, May 2010**  
**LOGIC DESIGN**

Duration : 3 Hours

Total Marks : 100

**Instructions :** 1) Answer 5 full questions at least one from each module.  
2) Assume any necessary data.

**MODULE – I**

1. a) A safe has 5 locks V, W, X, Y and Z all of which must be unlocked for the safe to open. The keys to the locks are distributed among 5 executives in the following manner.

Mr. A has keys for locks V and X

Mr. B has keys for locks V and Y

Mr. C has keys for locks W and Y

Mr. D has keys for locks X and Z

Mr. E has keys for locks V and Z.

5

- i) Determine the minimal number of executives required to open the safe.
- ii) Find all the combinations of executives that can open the safe, write an expression  $f(A, B, C, D, E)$  which specifies when the safe can be opened as a function of what executives are present.

iii) Who is the essential executive ?

- b) Perform the following :

8

i)  $(11.75)_{10}$  to Binary

ii)  $(8BF4)_{16}$  to octal

iii)  $(6327.4051)_8$  to decimal

iv)  $(675.625)_{10}$  to hexadecimal.

- c) Show that Dual of EX-OR is same as its complement.

4

- d) Prove the following using Boolean Algebra

$$A + \overline{A}B + A\overline{B} = A + B.$$

3

P.T.O.



2. a) For the following function find the essential prime implicants and prime implicants using QM method  $f(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5)$ .  
Realize the logic circuit using NAND gates only. 8
- b) Represent the decimal number.  $(358)_{10}$  in binary form using.  
i) Excess - 3 code ii) Gray code  
iii) Straight binary code iv) Octal code. 4
- c) Perform the following using 2's complement method  
i)  $48 - 23$  ii)  $48 - (-23)$   
iii)  $-48 - 23$  iv)  $23 - 48$  8

## MODULE - II

3. a) What is a T flipflop ? Explain with the help of a truth table and convert T flipflop to D flipflop. What is 'T' in a T flipflop ? 6
- b) What do you mean by master slave JK flipflop ? Explain why master slave flipflop is called a pulse triggered flipflop. 7
- c) Differentiate between combinational circuit and sequential circuit. Explain working of half subtract or using suitable diagram and truth table. 7
4. a) Design a 2 bit comparator. List all possible combinations and comparison support for your answer with a logic circuit. 5
- b) Design a combination circuit that operates as follows when the control signal enable = 1 m EX-OR gates shall be connected to implement a binary to gray code conversion. For enable = 0 the same EX-OR gates shall execute a gray code to binary conversion. 6
- c) What is the difference between a excitation table and truth table of a flipflop ? Give examples. 5
- d) Implement the following function using a multiplexer  
 $F(W, X, Y, Z) = \sum m(1, 2, 6, 7, 9, 11, 12, 14, 15)$ . 4

## MODULE - III


5. a) What is a Random counter ? Explain the working of 5 bit twisted ring counter with the help of diagrams. 6
- b) Design a 3 bit binary counter which counts according to the gray code use T flipflops. Explain its working. 8



- c) The binary number 1101 is serially entered (right most bit first) into a 4 bit parallel out shift register that is initially clear. What are the Q outputs after 2 clock pulses ?

6


6. a)

 

In figure  $A = 1$ ,  $B = 0$ ,  $C = 0$  and  $D = 1$ . After 3 clock pulses what are the data outputs.

- b) Design a synchronous counter using SR flipflops that goes through the following states.

8

 

- c) State the relative advantages and disadvantages of Asynchronous counters over synchronous counter.

5

#### MODULE – IV

7. a) Explain the terms state table, state reduction and state assignment with the help of examples.

5

- b) Explain the following :

- i) Registered PAL's      ii) Configurable PAL's.

5




- c) For the following state table design a sequential circuit using T flipflops after possible reduction.

10

Present State	Next State		O/P	
	x = 0	x = 1	x = 0	x = 1
a	f	b	0	0
b	d	c	0	0
c	f	c	0	0
d	g	a	1	0
e	d	c	0	0
f	f	b	1	1
g	g	h	0	1
h	g	a	1	0

8. a) Design a sequential circuit using SR flipflop :

8

 

- b) A combinational circuit is defined by the functions

$$F_1(A, B, C) = \Sigma(3, 5, 6, 7), F_2(A, B, C) = \Sigma(0, 2, 4, 7)$$

Implement the circuit with a PLA having 3 inputs, 4 product terms and 2 outputs.

7

- c) List and explain features of

i) 82S200 PLA

ii) 82S100 FPLA

5