



COMP 3 – 5 (RC)

S.E. (Comp.) (Semester – III) (RC) Examination, November/December 2015 LOGIC DESIGN

Duration : 3 Hours

Total Marks : 100

Instruction : Answer **any five** questions by selecting **atleast one** from **each** Module.

MODULE – I

1. a) Perform the following number conversion. 6
 - i) $(101011101)_2 \rightarrow \text{grey}$
 - ii) $(247.75)_{10} \rightarrow \text{hexadecimal}$
 - iii) $(3A.2F)_{16} \rightarrow \text{Decimal.}$
- b) Prove the following using Boolean algebraic theorems. 5
$$\overline{A}BC + A\overline{B}C + AB\overline{C} + ABC = AB + BC + CA$$
- c) Draw the logic diagram and construct the truth table for the following expression 4
$$X = A + B + \overline{CD}.$$
- d) What are self complementing codes ? Write two self complementing codes. 5
2. a) Realize the expression. 4
$$(A + C)(A + \overline{D})(A + B + \overline{C})$$
Using NOR gates only (2 inputs).
- b) Determine the single error correcting code for the binary data 1011 using even parity. 5
- c) For positive to negative logic system, what does an OR gate become and what does an AND gate become. 4
- d) Obtain the minimal sum of the product for the function 7
$$F(A, B, C, D) = \sum(1, 2, 3, 7, 8, 9, 10, 11, 14, 15)$$
by Quine Mcclusky method.

MODULE – II

3. a) What are combinational circuits ? Explain working of a full subtracter using suitable diagram, k-map and truth tables. 7
- b) Construct a 16 to 1 line multiplexer using only 2 to 1 line multiplexers. 7
- c) What master slave JK flip flop ? Explain why master slave flip flop is called a pulse triggered flip flop. 6

P.T.O.



4. a) Explain working of parallel adder. What are advantages and disadvantages over serial adder. 7
- b) Design a 2 bit comparator. List all possible combinations and comparison support for your answer with a logic circuit. 6
- c) What is the difference between an excitation table and truth table of a flipflop? Give example. 4
- d) Explain the advantages of edge triggered flip flop over level triggered flipflop. 3

MODULE – III

5. a) Explain the working of a serial in parallel out shift register with logic diagram and waveforms. 8
- b) Compare synchronous counter and asynchronous counter. Give examples with logic diagrams. 6
- c) With a neat diagram, explain the operation of a ring counter. Also sketch output waveform. 6
6. a) Explain how counter can be used as frequency divider. 6
- b) Design a 3 bit up/down counter which counts UP when the control signal $m = 1$ and counts down when $m = 0$. 7
- c) Design a mod-7 counter with asynchronous inputs for an up operation. Draw the output waveforms. 7


MODULE – IV

7. a) Explain the steps involved in design procedure for synchronous sequential circuits. 7
- b) A sequential circuit has 3 D-flip flops A, B, C and one input X. It is described by following flip flop input function 8
- $$DA = (BC' + B'C)X + (BC + B'C')X'$$
- $$DB = A$$
- $$DC = B$$
- i) Derive the state table for the circuit.
- ii) Draw two state diagram one for $X = 0$ and other for $X = 1$.
- c) Differentiate between PAL and FPAL. 5



8. a) Design a sequential circuit using SR flip flop.

8

 

- b) What are finite state machines ? Explain state table, state diagram and excitation table of R-S flip flop.
- c) Explain the architecture of PLA with the help of a block diagram.

6

6