

18-6-15 (M)



COMP – 3-5 (RC)

S.E. (Comp.) (Semester – III) (RC) Examination, May/June 2015
LOGIC DESIGN

Duration : 3 Hours

Total Marks : 100

- Instructions :** 1) Answer **five full** questions by selecting atleast **one** question from **each** Module.
2) Diagrams must be drawn **neat and clear with pencil only**.
3) **Assume** missing data if **necessary**.

MODULE – I

1. a) Perform the following number conversions : 6
i) $(630.25)_{10} \rightarrow (A)_2$
ii) $(A)_2 \rightarrow (B)_8$
iii) $(B)_8 \rightarrow (C)_{16}$
b) Reduce the Boolean expression using Boolean algebra. 4
$$\bar{A}B\bar{D} + \bar{A}B\bar{C}D + AB + \bar{A}BCD = B(A + \bar{C}).$$

c) Subtract the following decimal numbers by representing them in 8 bit using 2's complement method. 6
i) $(-57) - (+33)$
ii) $(+39) - (-21)$
iii) $(-17) - (-33).$
d) Why NAND and NOR gates are called as universal gates ? Explain using suitable diagrams. 4
2. a) Realize the following Boolean function : 6
$$Y = \bar{A}B + (C + \bar{D})E$$

Using : i) Two input NOR gates only
ii) Two input NAND gates only.

P.T.O.

COMP – 3-5 (RC)

-2-



- b) Represent $(-27)_{10}$ in 8 bit 3
- i) Sign magnitude form
 - ii) Sign 1's complement form
 - iii) Sign 2's complement form.
- c) A secure communication medium is used to transmit data to Bob by Alice. During the communication the data received by Bob was 1100100. Bob was in a dilemma to decide if the data sent was accurate or not. Suggest a secure technique using even numbering concept by which Bob can identify as well as correct the error involved if any. 4
- d) Find canonical sop expression of Boolean function 7
- $F(A, B, C, D) = ACD + \bar{A}\bar{C}D + BC + AB\bar{C}D + ABD$ and simplify using K-map.


MODULE – II

3. a) Design and explain the working of a 3 bit parallel adder/subtractor circuit. 8
- Use a control variable W and a circuit that functions as a full adder when $W = 0$ and as a full subtractor when $W = 1$.
- b) Realize the Boolean expression using 8 : 1 MUX where B, C, D appear on select lines S_2, S_1, S_0 respectively. 5
- $F(A, B, C, D) = \sum m(1, 6, 7, 9, 10, 11, 12)$.
- c) Distinguish between combinational circuits and sequential circuits. 5
- d) Define code converters. 2
4. a) Explain the circuit diagram, state diagram, present state-next state table, excitation table and characteristic equation of S-R flip-flop. 6
- b) Realize J-K flip-flop using D flip-flop. 8
- c) Explain level triggered and edge triggered flip-flops with the help of timing diagrams. 6



MODULE – III

 5. a) Explain the steps involved in the design of synchronous counters. 6
- b) What do you mean by glitches or false spikes that appear at the decoding gate output in an asynchronous counter? Give any two ways by which it can be avoided. 6
- c) What are the different applications of counters? 4
- d) The content of 4 bit shift register is initially 1101. The contents of the register is shifted 4 times to the left with serial input being 101101. What is the content of the register after each shift? 4
6. a) Design a 3 bit Johnsons counter. Explain its working. 8
- b) Explain the following registers : 8
- i) SISO ii) SIPO
- iii) PISO iv) PIPO
- c) Consider the parallel in parallel out register shown below : 4



In figure, if $A = 1$, $B = 0$, $C = 1$, $D = 1$ are the initial contents given to the respective inputs of the flip flop. If a consistent input is given that is $A = 0$, $B = 1$, $C = 0$, $D = 1$ to the respective flip flop inputs. What will be the data output after the 3rd clock pulse?



MODULE – IV


7. a) Compare Moore circuit and Mealy circuit.

6

$$K = 1 + 2^{\mu}$$


- b) Obtain state table, state diagram and state equation for the circuit shown below :

6

 

- c) Design a circuit that will function as prescribed by the state diagram shown below. Use SR flip flops for implementation.

8

 

8. a) Implement PLA table for the following Boolean functions :

6

$$F_1(A, B, C) = \sum_m(0, 1, 6, 7)$$

$$F_2(A, B, C) = \sum_m(3, 6, 7)$$

$$F_3(A, B, C) = \sum_m(0, 1, 3, 7)$$

- b) How is FPLA architecture different from PAL ?

6

- c) Explain the following :

6

i) Registered PAL's

ii) Configurable PAL's.

- d) What does PAL 12L8 indicate ?

2