



F.E. Semester – II (RC) Examination, November/December 2015
BASIC ELECTRONICS ENGINEERING

Duration : 3 Hours

Total Marks :100

- Instructions :** 1) Answer **any five** questions selecting atleast **one** from **each** Module.
2) Make suitable assumption, **if required**.

MODULE – I

1. a) Draw a forward biased Pn junction and explain the following terms :
 - i) Potential Barrier
 - ii) Reverse saturation current.


6
- b) Draw the V-I characteristics of a Pn junction diode and show how the dynamic resistance of the diode can be determined.

4
- c) Explain the piecewise linear equivalent circuit of a diode and draw its corresponding V-I characteristics.

5
- d) What is transition capacitance of a diode ? Give its application.

5
2. a) Find V_0 and I for the given network.

3

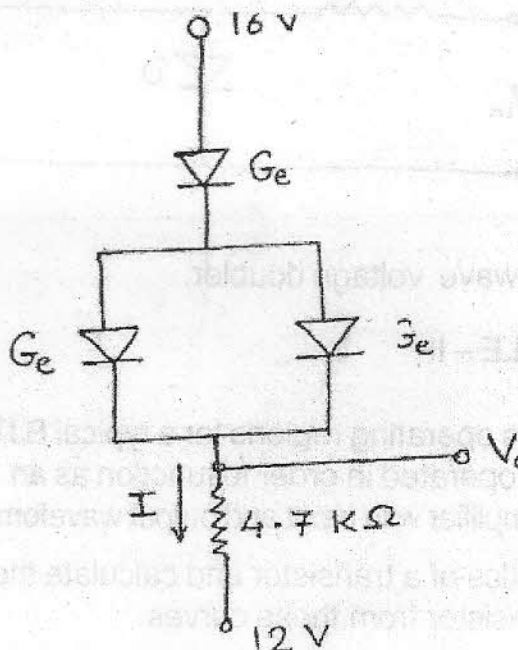


- b) Derive the rms voltage of a Centre-tapped full wave rectifier.

3







- c) Determine the maximum and minimum values of zener diode current for the circuit shown below if zener has $V_z = 20\text{ V}$.

5

 

- d) Analyse the circuits given in the figures below and draw output waveforms. (Assume Ideal diodes and large R_L)

6

    

- e) Draw diagram and waveform of fullwave voltage doubler.

3


MODULE – II

3. a) Explain the construction and various operating regions for a typical BJT. In which region should a transistor be operated in order to function as an amplifier? Draw the circuit of a CE amplifier with input and output waveforms. 10
- b) Sketch typical CB input characteristics of a transistor and calculate the input dynamic resistance of the transistor from these curves. 5
- c) Why are limits of operation required in a transistor? What are the necessary conditions required to be fulfilled for the proper operation of a CE transistor? 5



4. a) In the following biasing circuit, a supply of 6V and a load resistance of $1\text{ K}\Omega$ is used.
- Find the value of R_B so that a Ge transistor with $\beta = 20$ and $I_{CBO} = 2\text{ }\mu\text{A}$ draws an I_C of 1mA.
 - What I_C is drawn if the transistor parameters change to $\beta = 25$ and $I_{CBO} = 10\text{ }\mu\text{A}$ due to rise in temperature ?

6

 

- Show how the emitter bias circuit helps in stabilizing the Q – point with respect to temperature and β variations.
- Prove mathematically that the operating point in a potential divider biasing circuit is independent of β .

8


6

MODULE – III

5. a) Explain the basic construction of a n-channel JFET.
Apply the proper drain to source voltage and sketch the depletion region for $V_{GS} = 0$ and V_{DS} at some positive voltage.
- b) For fixed biased configuration given below, determine I_{DQ} , V_{DS} and V_{GSQ} .

7


6

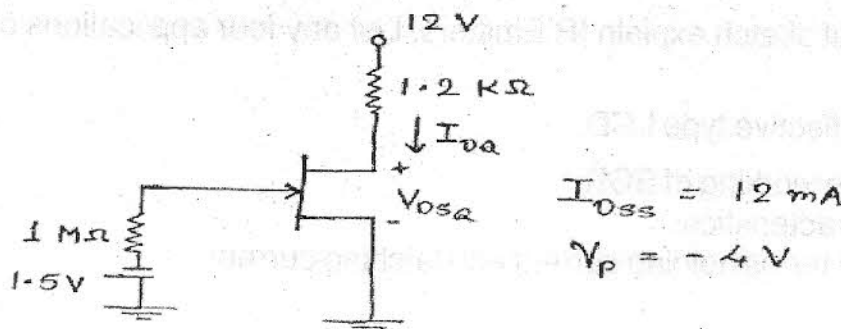



c) With neat diagrams and set of equations explain the self bias configuration of JFET. 7

 6. a) Determine I_{DQ} , V_{GSQ} and V_{DS} for the network shown below : 8



b) Draw and explain output characteristics and transfer characteristic curve for P – channel depletion type MOSFET. Show how can transfer characteristics be obtained from output characteristics. 7

c) Explain with neat diagram the basic CMOS operation. 5

MODULE – IV

7. a) Describe various methods of transistor fabrication. 6

b) Describe the OPAMP operation for double ended output with single ended input. 6

c) Draw a Wein Bridge Oscillator and write the expression for frequency of oscillation. 3

d) Explain the feedback concept with a simple block diagram. 5

8. a) With a neat sketch explain IR Emitters. List any four applications of IR emitters. 6

b) Explain reflective type LCD. 6

c) Explain the working of SCR. 8

Draw characteristics.

Define the terms holding current and latching current.