

**S.E. (Computer) (Sem. – III) (RC) Examination, May/June 2012
INTEGRATED ELECTRONICS**


Duration : 3 Hours

Total Marks : 100

Instructions : 1) Answer **any five** questions, atleast **one** from **each** Module.
2) Make suitable assumptions, **wherever** necessary.

Module – 1

 1. a) List any characteristics that an ideal op-amp should exhibit. 5
b) What is 'negative feedback' ? And give its advantages. 5
c) Derive a equation for closed loop voltage gain for voltage – series feedback amplifier. 7
d) Why are compensating networks are required ? 3
2. a) Draw and explain integrator circuit and draw necessary waveforms. What do you mean by 'practical integrator' ? 7



In the above fig. if $\pm V_{sat} = \pm 10V$, find V_{UT} and V_{LT} of $V_i = 6 \sin \omega t$ find the waveform of the output voltage. Why Schmitt trigger is called as Regenerative comparator. 7

- c) With the help of neat circuit diagram and equations, explain the following :
 - 1) Summing amplifier
 - 2) Scaling amplifier
 - 3) Averaging amplifier.6



Module – 2

- | | | |
|-------|---|----|
| 3. a) | With the help of diagram, explain briefly series voltage regulator. | 4 |
| b) | Explain any two applications of timer 555 in detail. | 10 |
| c) | Draw functional block diagram of regulator IC 723. Explain the design of IC 723 as low voltage regulator, along with circuit diagram and equations. | 6 |
| 4. a) | Explain working of timer 555 in astable mode. Draw the circuit and derive necessary equations. | 7 |
| b) | Explain working principle and basic operation of PLL with the help of block diagram. | 5 |
| c) | Describe in detail any two applications of PLL. | 8 |

Module – 3

- | | | |
|-------|--|---|
| 5. a) | Draw the circuit diagram of a TTL gate with Totem – pole output driver and explain its operation. What is the use of clamping diodes in TTL gate ? | 8 |
| b) | Compare the characteristics of following Digital IC logic families. | 6 |
| 1) | RTL | |
| 2) | DTL | |
| 3) | HTL | |
| c) | Explain the operation of CMOS inverter gate and give one advantages of CMOS inverter. | 6 |
| 6. a) | Explain with diagram, working of RTL 2-input circuit. State its advantages and disadvantages. | 8 |
| b) | Define the following current and voltage parameters of digital IC | |
| 1) | Low level input voltage | |
| 2) | High level input voltage | |
| 3) | High level supply current | |
| 4) | Low level output current. | 4 |
| c) | Draw the circuit diagram of an ECL OR/NOR gate and explain its operation. Discuss why ECL is the fastest of all logic families. | 8 |



Module – 4

7. a) Define the following specification of A/D converter :
- 1) digital output format
 - 2) Input impedance. 2
- b) A 8-bit weighted resistor DAC produces an O/P voltage of 2.0 V for an i/p of 00110110. What will be value of V_{out} for an input code.
- 1) 11000001 8
 - 2) 00011100. 8
- c) Explain an ADC using voltage to frequency conversion. Sketch necessary output waveforms. 8
- d) A D/A converter has a full scale analog output of 10 V and accepts 6 binary bits as input. Find the voltage corresponding to each analog step. 2
8. a) Draw the circuit diagram of 4-bit R-2R binary ladder D/A converter. Given logic '1' = 10 V and logic '0' = 0 V, $R_F = 10\text{ k}\Omega$, $R = 10\text{ k}\Omega$. Calculate the output voltages, when input are
- 1) 1001
 - 2) 1100. 6
- b) Explain the working of successive approximation A/D converter, with a diagram. 8
- c) A 4-bit DAC is shown in below fig. and has its logic levels given by $V_{high} = 5\text{V}$ and $V_{low} = 0\text{V}$. Calculate the o/p voltages when digital inputs DCBA are given by
- 1) 1011 6
 - 2) 1010.

