

Sem - III in Regular 23/12/13
comp part



COMP 3 - 6 (RC)

S.E. (Computer) (Semester - III) (RC) Examination, Nov./Dec. 2013
INTEGRATED ELECTRONICS

Duration : 3 Hours


Total Marks : 100

- Instructions : 1) Attempt any five, choosing at least one from each Module.
2) Assume any data, if necessary.


MODULE - 1

1. a) Calculate the CMRR for the circuit measurement shown in fig.

5

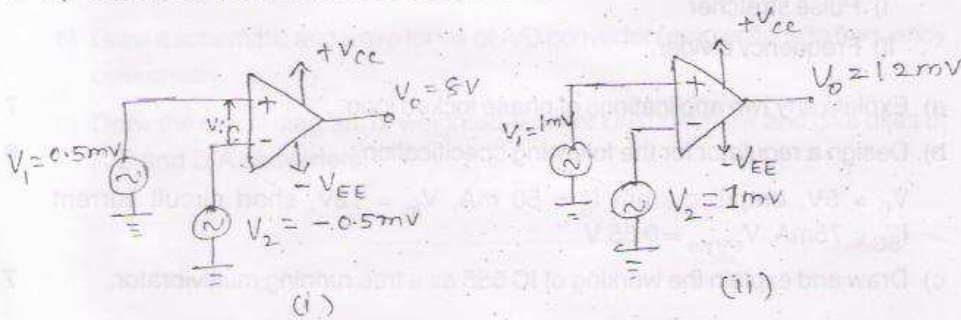

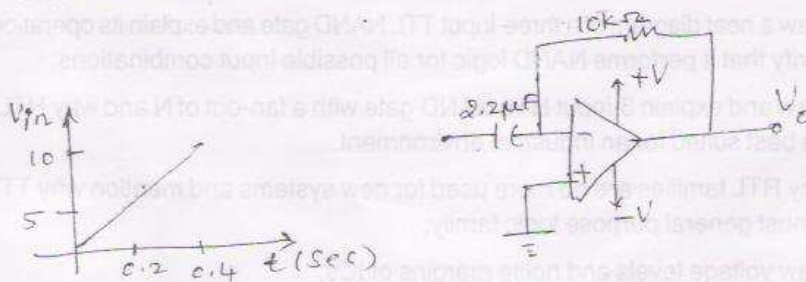- b) Explain the working of a zero crossing detector. 5
c) With a neat circuit diagram describe the operation of a non-inverting op-amp summer and averager with three inputs. 6
d) Draw the block schematic of an op-amp and describe the operation of each block. 4
2. a) For the differentiator circuit shown in fig. determine the output voltage, if the input goes from 0 V to 10 V in 0.4 seconds. Assume the input voltage changes at constant rate. 4



P.T.O.




- b) Draw the circuit diagram and explain the working of an op-amp configured in the inverting mode as a summing, scaling and averaging amplifier. 8
- c) Draw and explain the working of a Schmitt trigger. 8

MODULE – 2

3. a) Describe the operating principle of PLL. 6
- b) Give pin description of LM 105 with its block diagram. 6
- c) Write a short note on 8
- i) Pulse stretcher
- ii) Frequency divider.
4. a) Explain any two applications of phase locked loop. 7
- b) Design a regulator for the following specification : 6
- $V_0 = 5V$, output current $I_0 = 50 \text{ mA}$, $V_{in} = 12V$, short circuit current $I_{SC} = 75\text{mA}$, $V_{sense} = 0.65 \text{ V}$.
- c) Draw and explain the working of IC 555 as a free running multivibrator. 7

MODULE – 3

 5. a) List the characteristics of CMOS and name the types in bipolar and unipolar logic families. 6
- b) Explain the working of two input DTL NAND gate and draw the circuit for three input modified DTL gate. 8
- c) Mention the fastest logic family and give its disadvantages along with a symbol for a 3-input OR/NOR gate. 6
6. a) Draw a neat diagram of a three-input TTL NAND gate and explain its operation. Verify that it performs NAND logic for all possible input combinations. 8
- b) Draw and explain 3-input HTL NAND gate with a fan-out of N and why HTL are best suited for an industrial environment. 6
- c) Why RTL families are no more used for new systems and mention why TTL is most general purpose logic family. 4
- d) Draw voltage levels and noise margins of ICs. 2



MODULE – 4

7. a) Explain the specifications of D/A converters. 8
- b) Describe 3-bit binary Ladder D/A network. State its advantages and disadvantages. 7
- c) An 8-bit successive approximation A/D converter has a resolution of 20 mV. If the analog input voltage is 1.085 V, find its digital output in binary form. 5
8. a) Illustrate how output of counter in dual-slop A/D converter is proportional to the analog voltage. 6
- b) Draw a schematic and wave forms of A/D converter using voltage to frequency conversion. 6
- c) Draw the circuit diagram of weighted-resistor D/A converter and give uses of A/D and D/A converters. 8
-